

---

# **ECE 4514**

## **Digital Design II**

### **Spring 2008**

## **Lecture 6:**


# **A Random Number Generator in Verilog**

*A Design Lecture*

Patrick Schaumont

# What is a random number generator?

---

 

# What do I do with randomness?

---

- ❑ Play games!

- Have the monsters appear in different rooms every time

- ❑ Do statistical simulations

- Simulate customers in a shopping center (find the best spot for a new Chuck E Cheese)

- ❑ Run security protocols


- Make protocol resistant against replay

- ❑ Encrypt documents

- Use random numbers as key stream

# Encrypt Documents

---

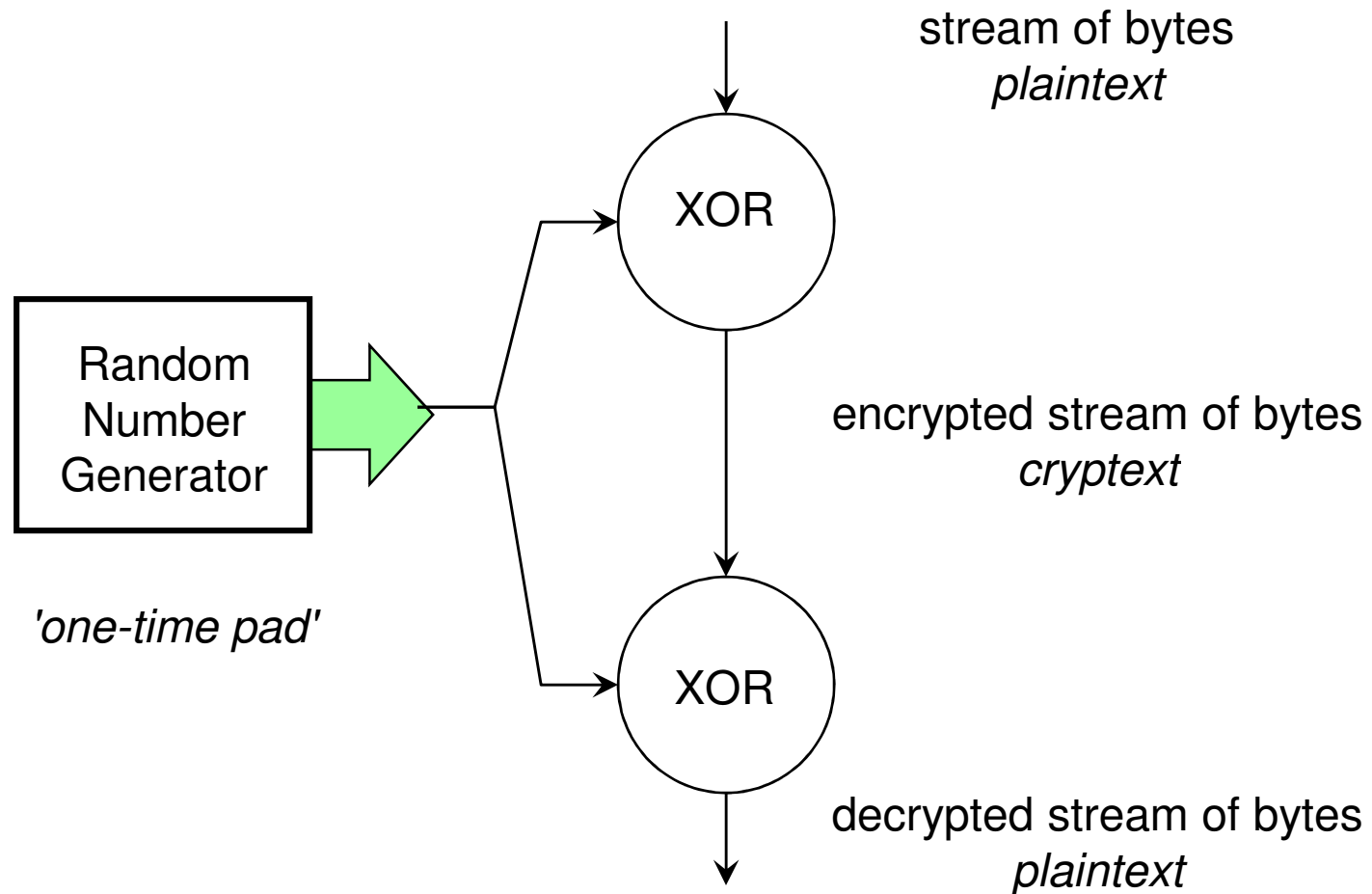

# Random numbers by physical methods

- ❑ Use dice, coin flips, roulette
- ❑ Use thermal noise (diodes and resistors)
- ❑ Use clock jitter (use ring oscillators)
- ❑ Use radioactive decay
- ❑ Use Lava Lamps
  - Patented!

**United States Patent** [19]  
Noll et al.



US005732138A

[11] **Patent Number:** **5,732,138**  
[45] **Date of Patent:** **Mar. 24, 1998**

[54] **METHOD FOR SEEDING A PSEUDO-RANDOM NUMBER GENERATOR WITH A CRYPTOGRAPHIC HASH OF A DIGITIZATION OF A CHAOTIC SYSTEM**

[75] **Inventors:** **Landon Curt Noll; Robert G. Mende,**  
both of Sunnyvale; **Sanjeev Sisodiya,**  
Mountain View, all of Calif.

[73] **Assignee:** **Silicon Graphics, Inc.,** Mountain View,  
Calif.

[21] **Appl. No.:** **592,891**

[22] **Filed:** **Jan. 29, 1996**

[51] **Int. CL.<sup>6</sup>** ..... **H04L 9/22**

[52] **U.S. Cl.** ..... **380/28; 380/46; 364/717**

[58] **Field of Search** ..... **380/14, 28, 46;**  
**395/421.06; 364/717**

[56] **References Cited**

4,780,816 10/1988 O'Connell ..... 395/421.06  
4,951,314 8/1990 Shreve ..... 380/14  
4,964,162 10/1990 McAdam et al. .... 380/14  
5,048,086 9/1991 Bianco et al. .... 380/28

*Primary Examiner*—Salvatore Cangialosi

*Attorney, Agent, or Firm*—Wagner, Murabito & Hao

[57] **ABSTRACT**

A method for generating a pseudo-random numbers Initially, the state of a chaotic system is digitized to form a binary string. This binary string is then hashed to produce a second binary string. It is this second binary string which is used to seed a pseudo-random number generator. The output from the pseudo-random number generator may be used in forming a password or cryptographic key for use in a security system.

# Random numbers by computational methods

---

- ❑ Not truly random, but *pseudo* random
  - meaning, after some time the same sequence returns
- ❑ Linear Congruential Generator

$$x(n+1) = [ a.x(b) + b ] \text{ mod } m$$

Eg.  $a = 15, b = 5, m = 7$

*a, b, m must be chosen carefully!  
for a maximum length sequence*

$$X(0) = 1$$

$$X(1) = (15 + 5) \text{ mod } 7 = 6$$

$$x(2) = (15*6 + 5) \text{ mod } 7 = 4$$

$$x(3) = 2$$

$$x(4) = 0$$

$$x(5) = 5$$

$$x(6) = 3$$

$$x(7) = 1$$

$$x(8) = \dots$$

# A quick way to generate random numbers

---

- ❑ Verilog has a builtin random number generator


```
module random(q);  
    output [0:31] q;  
    reg [0:31] q;  
  
    initial  
        r_seed = 2;  
  
    always  
        #10 q = $random(r_seed);  
endmodule
```

- ❑ Nice, but only for testbenches ...
- ❑ Instead, we want an hardware implementation

# Linear Feedback Shift Register

---
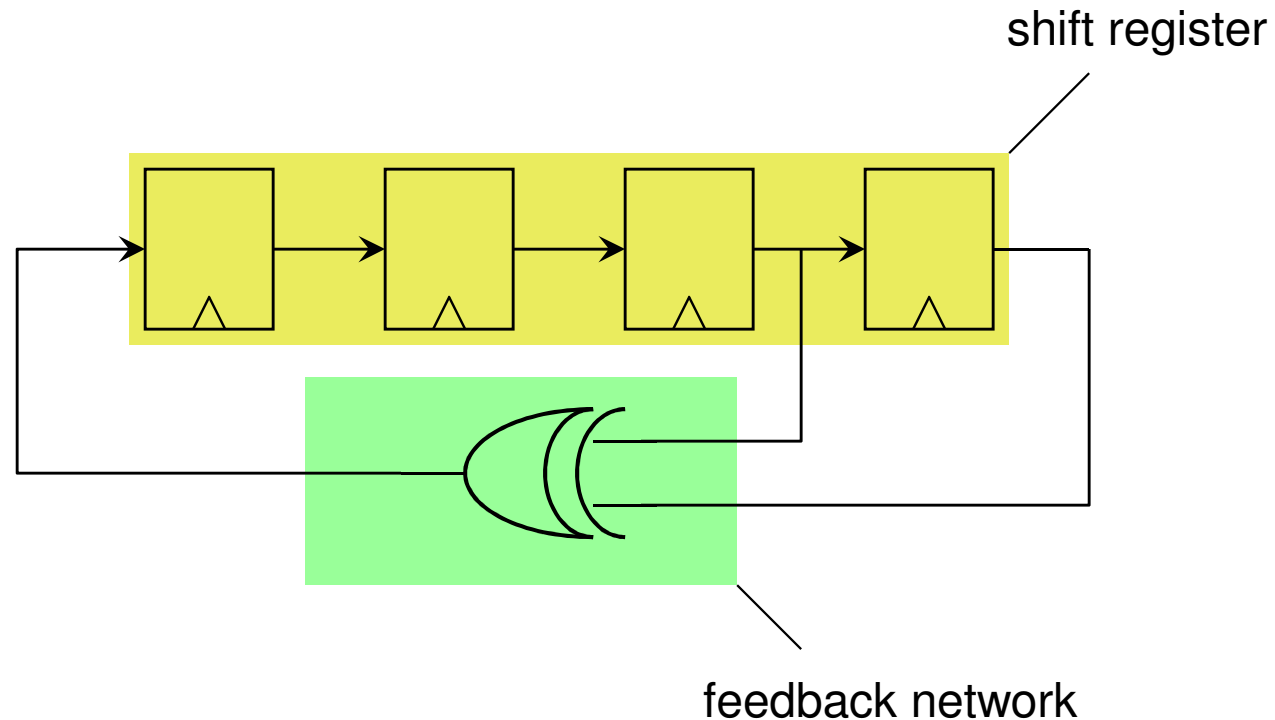
## ❑ Pseudo Random Numbers in Digital Hardware






# Linear Feedback Shift Register

---


- ❑ All zeroes
  - not very useful ...

 

# Linear Feedback Shift Register

---


- ❑ Non-zero state is more interesting

 

# Linear Feedback Shift Register

---

- ❑ Non-zero state is more interesting

 


10

# Linear Feedback Shift Register

---

- ❑ Non-zero state is more interesting

 


100

# Linear Feedback Shift Register

---

- ❑ Non-zero state is more interesting

 


1001

# Linear Feedback Shift Register

---

- ❑ Non-zero state is more interesting

 


10011

# Linear Feedback Shift Register

---

- ❑ Non-zero state is more interesting

 


100110

# Linear Feedback Shift Register

---

- ❑ Non-zero state is more interesting

 

1001101


etc ...


 
# Linear Feedback Shift Register

---



- This is actually a finite state machine


  
# Linear Feedback Shift Register

---



- This is actually a finite state machine



**How many states will you see?**

# Linear Feedback Shift Register


□ 15 states

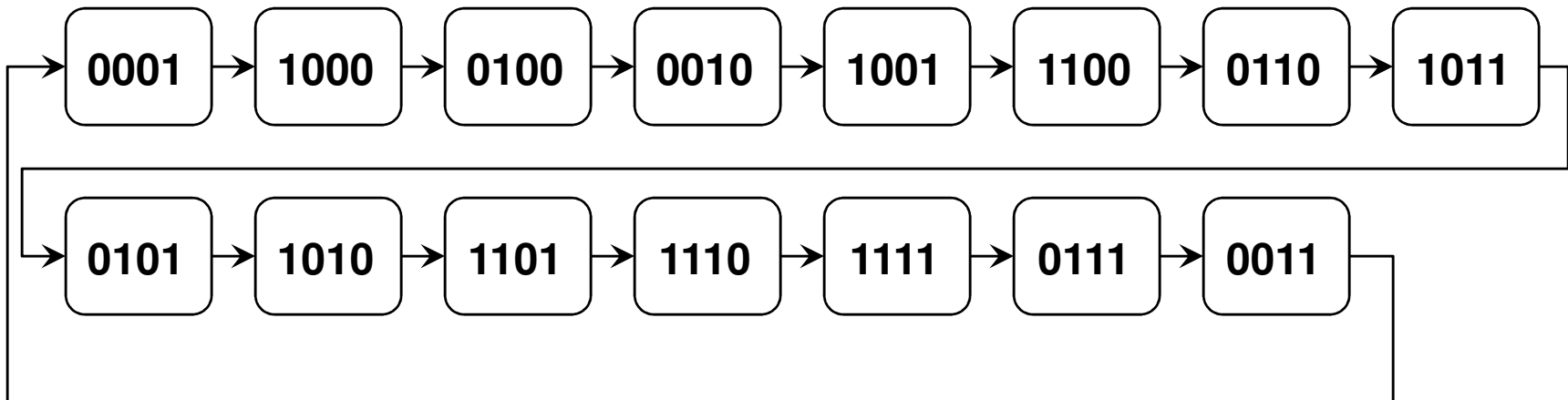 
 
# Linear Feedback Shift Register

---

- We can specify an LFSR by means of the *characteristic polynomial* (also called feedback polynomial)



$$P(x) = x^4 + x^3 + 1$$

There exists elaborate finite-field math to analyze the properties of an LFSR - outside of the scope of this class

# Linear Feedback Shift Register

---

- So, knowing the polynomial you can also draw the LFSR

$$P(x) = x^8 + x^6 + x^5 + x^4 + 1$$

How many taps ?

How many 2-input XOR?

# Linear Feedback Shift Register


---

- So, knowing the polynomial you can also draw the LFSR

$$P(x) = x^8 + x^6 + x^5 + x^4 + 1$$

How many taps ? 8

How many 2-input XOR?

 


# Linear Feedback Shift Register

- So, knowing the polynomial you can also draw the LFSR

$$P(x) = x^8 + x^6 + x^5 + x^4 + 1$$

How many taps ? 8

How many 2-input XOR? 3

 

# Linear Feedback Shift Register

---

- ❑ Certain polynomials generate very long state sequences. These are called maximal-length LFSR.


$P(X) = x^{153} + x^{152} + 1$   
is a maximum-length feedback polynomial

State machine with  $2^{153} - 1$  states ..


 
# Fibonacci and Galois LFSR


- ❑ This format is called a Fibonacci LFSR



Fibonacci  
~1175-1250



 - ❑ Can be converted to an equivalent Galois LFSR




Evariste  
Galois  
1811-1832


 
# Fibonacci and Galois LFSR

---


- ❑ Each Fibonacci LFSR can transform into Galois LFSR:
  - Reverse numbering of taps
  - Make XOR inputs XOR outputs and vice versa
  
- ❑ Example: starting with this Fibonacci LFSR


 
# Fibonacci and Galois LFSR

---


- ❑ Disconnect XOR inputs
- ❑ Reverse tap numbering (not the direction of shifting!)


 
# Fibonacci and Galois LFSR


---

- Turn XOR inputs into XOR outputs and vice versa




# Which one is better for digital hardware?

## ❑ Fibonacci

 


## ❑ Galois

 


# Which one is better for digital hardware?

## ❑ Fibonacci

 

 
## ❑ Galois computes all taps in parallel




# Which one is better for software?

## ❑ Fibonacci

 


## ❑ Galois

 


# Which one is better for software?

## ❑ Fibonacci

 
 
## ❑ Galois


```
char_v = (char_v >> 1) ^ (-(signed char) (char_v & 1) & 0xe)
```






# Let's write an LFSR in Verilog

---

 

xor(out, in1, in2)

 

You need to build this one  
(structural, behavioral)

# A Flip flop

---

```
module flipflop(q, clk, rst, d);  
    input clk;  
    input rst;  
    input d;  
    output q;  
    reg q;  
  
    always @(posedge clk or posedge rst)  
        begin  
            if (rst)  
                q = 0;  
            else  
                q = d;  
            end  
        endmodule
```

# A Flip flop

---

## ❑ Setup Time:

- Time D has to be stable before a clock edge

## ❑ Hold Time:

- Time D has to be stable after clock edge

## ❑ Propagation Delay:

- Delay from clock edge to Q
- Delay from reset to Q

**How to specify propagation delay ?**

# A Flip flop

---

```
module flipflop(q, clk, rst, d);  
    input clk;  
    input rst;  
    input d;  
    output q;  
    reg q;  
  
    always @(posedge clk or posedge rst)  
        begin  
            if (rst)  
                q = 0;  
            else  
                q = d;  
            end  
        endmodule
```

**How to specify propagation delay ?**

# A Flip flop

---


```
module flipflop(q, clk, rst, d);  
    input clk;  
    input rst;  
    input d;  
    output q;  
    reg q;  
  
    always @(posedge clk or posedge rst)  
        begin  
            if (rst)  
                #2 q = 0;  
            else  
                q = #3 d;  
            end  
  
    specify  
        $setup(d, clk, 2);  
        $hold(clk, d, 0);  
    endspecify  
endmodule
```

*Test setup, hold*  
*See Chapter 10*  
*Palnitkar*

# Let's turn the LFSR into a module


---

How to program this?

 


# Let's turn the LFSR into a module

---

 

# Multiplexer symbol

---

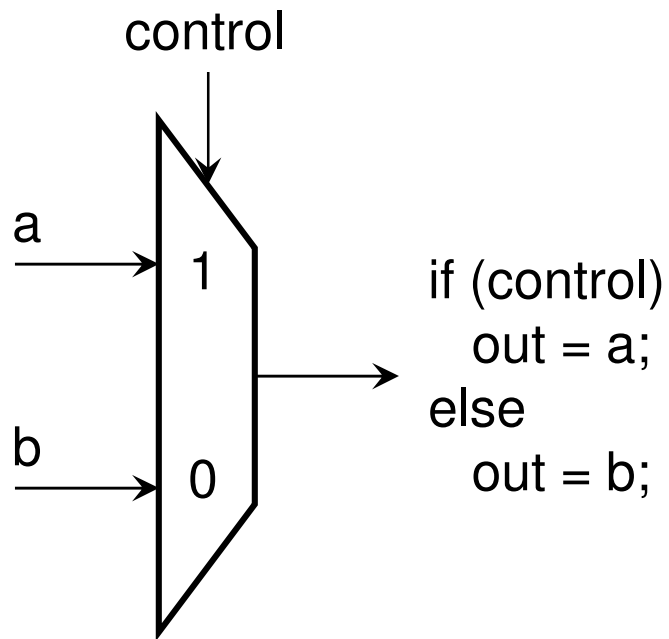


bit multiplexer

```
module mux(q, control, a, b);  
  output q;  
  reg q;  
  input control, a, b;  
  
  wire notcontrol;  
  
  always @(control or  
           notcontrol or  
           a or b)  
    q = (control & a) |  
        (notcontrol & b);  
  
  not (notcontrol, control);  
endmodule;
```




# LFSR, structural

 


```
module lfsr(q, clk, rst, seed, load);  
    ...  
    wire [3:0] state_out;  
    wire [3:0] state_in;  
  
    flipflop F[3:0] (state_out, clk, rst, state_in);  
  
endmodule
```

# LFSR, structural

 

```
module lfsr(q, clk, rst, seed, load);  
    ...  
    wire [3:0] state_out;  
    wire [3:0] state_in;  
    wire nextbit;  
  
    xor G1(nextbit, state_out[2], state_out[3]);  
  
    assign q = nextbit;  
  
endmodule
```

# LFSR, structural

 

```

module lfsr(q, clk, rst, seed, load);
    ...
    wire [3:0] state_out;
    wire [3:0] state_in;
    wire nextbit;

    mux M1[3:0] (state_in, load, seed, {state_out[2],
                                         state_out[1],
                                         state_out[0],
                                         nextbit});

    assign q = nextbit;
endmodule

```

# LFSR module - complete

---

```
module lfsr(q, clk, rst, seed, load);
    output q;
    input [3:0] seed;
    input load;
    input rst;

    wire [3:0] state_out;
    wire [3:0] state_in;

    flipflop F[3:0] (state_out, clk, rst, state_in);
    mux M1[3:0] (state_in, load, seed, {state_out[2],
                                         state_out[1],
                                         state_out[0],
                                         nextbit});
    xor G1(nextbit, state_out[2], state_out[3]);
    assign q = nextbit;

endmodule
```

# LFSR testbench

---

```
module lfsrtst;
    reg clk;
    reg rst;
    reg [3:0] seed;
    reg load;
    wire q;
    lfsr L(q, clk, rst,
          seed, load);


    // initialization
    // apply reset pulse
    initial
        begin
            clk = 0;
            load = 0;
            seed = 0;
            rst = 0;
            #10 rst = 1;
            #10 rst = 0;
        end
end
```

```
        // drive clock
        always
            #50 clk = !clk;

        // program lfsr
        initial begin
            #100 seed = 4'b0001;
                load = 1;
            #100 load = 0;
        end


endmodule
```

# Simulation ..

 


# Synthesis ..

---

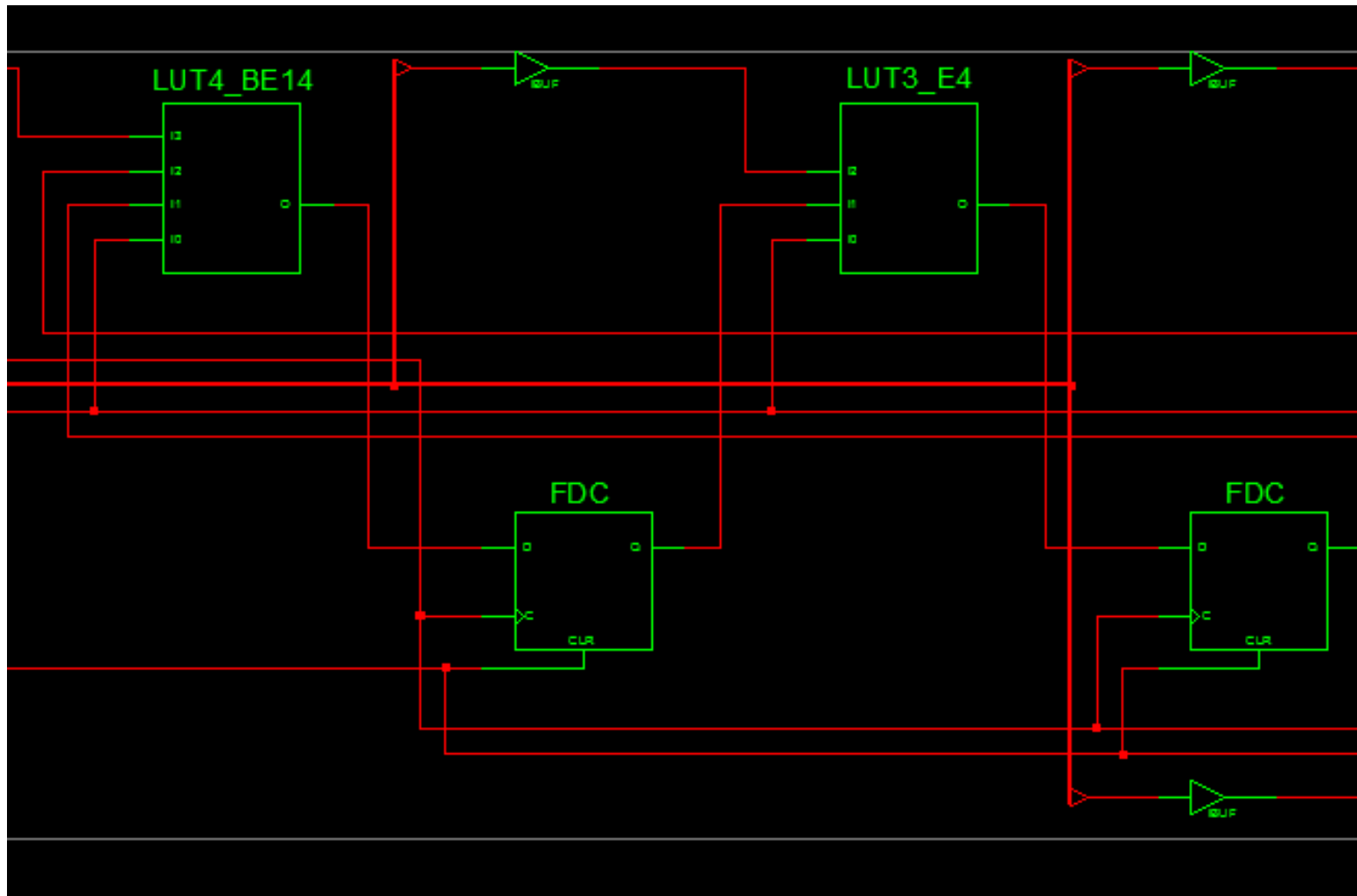

# Place and Route ..

---

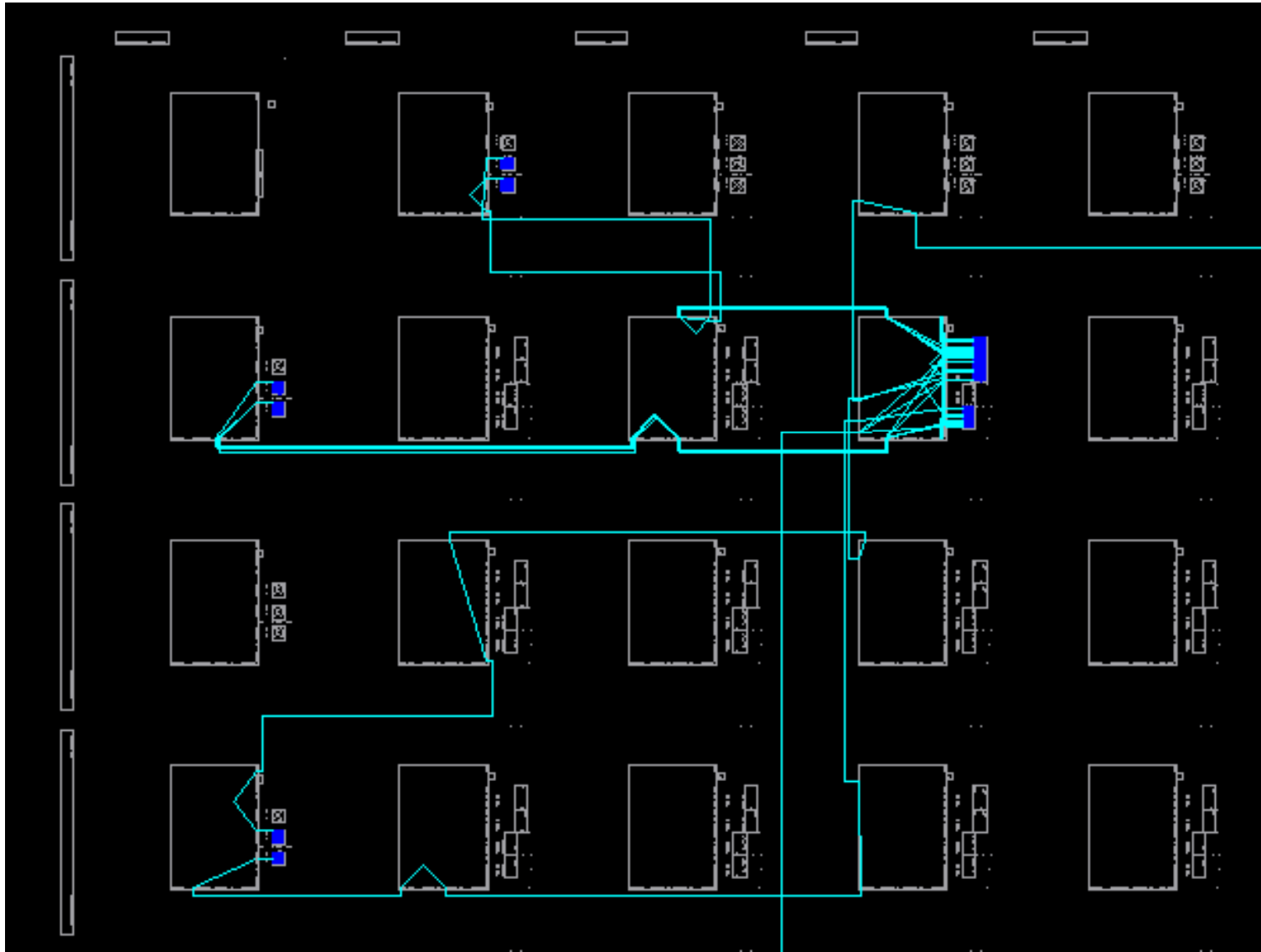





# Can a random number generator have flaws?

## ❑ Problem #1: it can have bias

- Meaning: a certain number occurs more often than others
- Expressed in the *entropy rate* of the generator
- Entropy = true information rate (in bit/sec), can be lower than the actual bitrate of the random number generator
- Example: Assume an RNG that produces three events A,B,C encoded with two bits

	symbol	probability	bitpattern
RNG	A	$P(A) = 1/2$	00
	B	$P(B) = 1/4$	01
	C	$P(C) = 1/4$	10

E.g. ABACAABC... is encoded as 0001001000000110...

So this bitstream has much more '0' than '1'. It has a bias.

# Can a random number generator have flaws?

## ❑ Problem #1: it can have bias

- Meaning: a certain number occurs more often than others
- Expressed in the *entropy rate* of the generator
- Entropy = true information rate (in bit/sec), can be lower than the actual bitrate of the random number generator
- Example: Assume an RNG that produces three events A,B,C encoded with two bits

		symbol	probability	<b>better bitpattern</b>
RNG	↗	A	$P(A) = 1/2$	<b>0</b>
	→	B	$P(B) = 1/4$	<b>10</b>
	↘	C	$P(C) = 1/4$	<b>11</b>

E.g. ABACAABC... is encoded as 010011001011...

In this bitstream, the number of '1' and '0' are balanced.

# Can a random number generator have flaws?

---

- ❑ Problem #1: it can have bias
  - Do LFSR have a bias ?

# Can a random number generator have flaws?

---

## ❑ Problem #1: it can have bias

- Do LFSR have a bias ?
- Yes, they have a small bias because the all-zero state never appears.
- However, for a very long LFSR, the bias becomes negligible

# Can a random number generator have flaws?

---


## ❑ Problem #2: it can be predicted

- Not when truly random physical phenomena
- But, if it is a Pseudo RNG (like an LFSR), it is a deterministic sequence.
- Is this really a problem? Yes!
  - Don't want to use a predictable RNG for dealing cards, driving a slot machine, ... (at least not if you own the place).
  - Don't want to use predictable RNG in security. Predictability = weakness

# Can a random number generator have flaws?
 
## ❑ Problem #2: it can be predicted

- The real issue for PRNG is: can the value of bit  $N+1$  be predicted when someone observes the first  $N$  bits.



## LFSR are *very* predictable ..

---

- ❑ Predicting the next output bit is equivalent to knowing the feedback pattern of the LFSR and the states of all LFSR flip-flops.
- ❑ Mathematicians (Berlekamp-Massey) found that:
  - Given an N-bit LFSR with unknown feedback pattern, then only  $2N$  bits are needed to predict bit  $2N + 1$
- ❑ So let's say we have an 8-bit LFSR, then we need only 16 bits of the RNG stream before it becomes predictable
- ❑ **LFSR are *unsuited* for everything that should be unpredictable**




# To be unpredictable, the LFSR should be long

## ❑ Solution 1

Use a maximal-length  $P(x) = x^N + \dots + 1$   
with  $N \gg \gg$  (E.g. 65,536)


Very expensive to make! 64K flip-flops ..
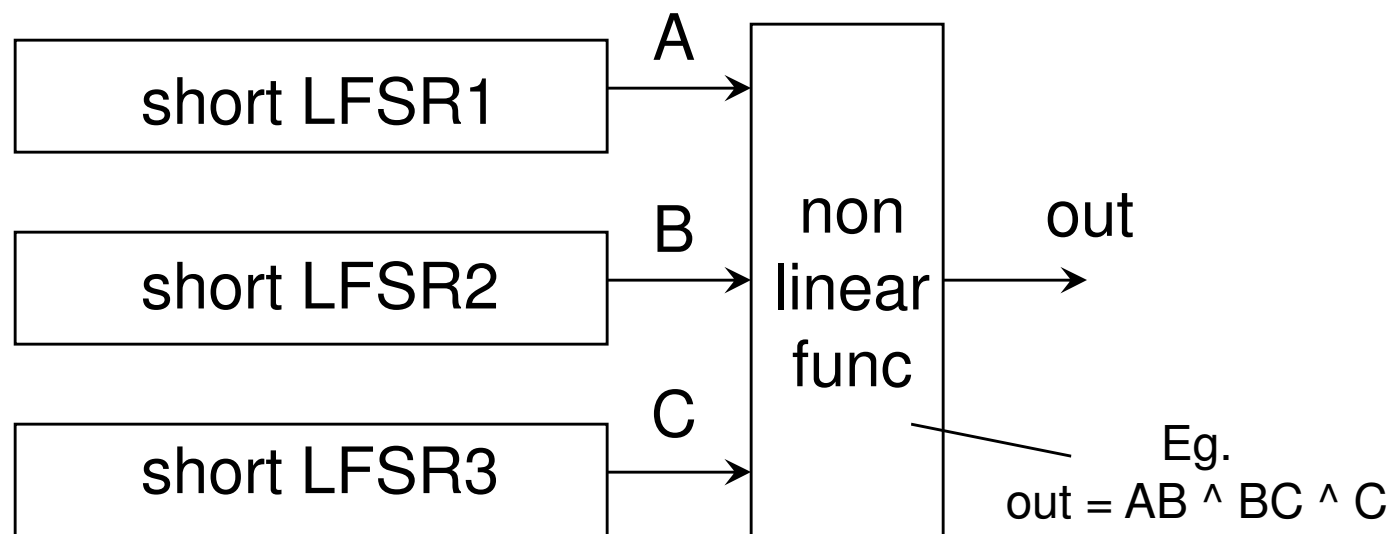
## ❑ Solution 2: Non-linear Combination Generator



# Example design by Tkacik, 2002

---

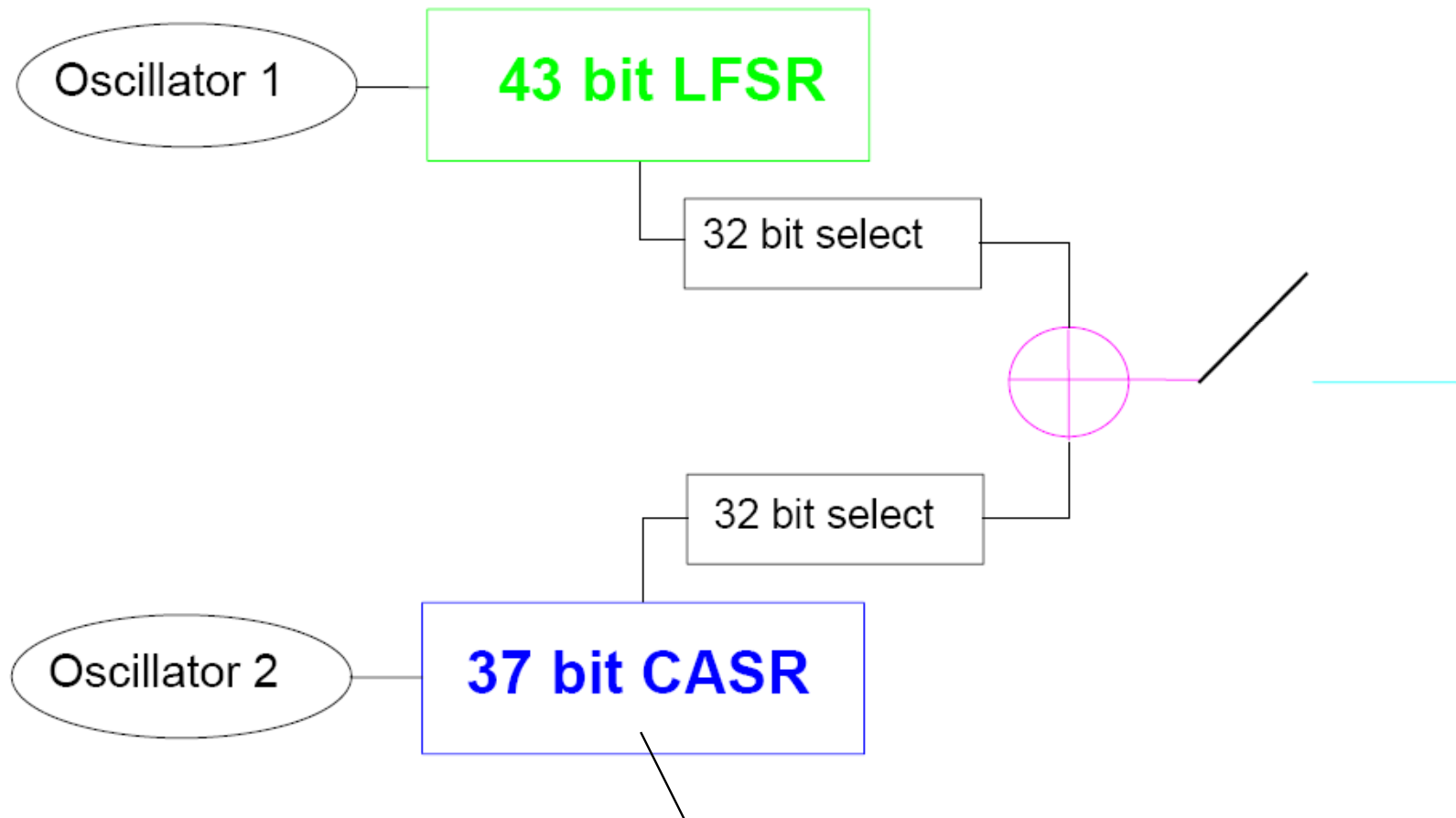

Cellular Automata Shift Register

# Example design by Tkacik, 2002


---

## ❑ 43-bit LFSR defined by

- $P(X) = X^{43} + X^{41} + X^{20} + X + 1 \Rightarrow 3\text{XOR}, 43 \text{ taps}$
- Maximal Length:  $2^{43}-1$
- Bias  $\sim 2^{-43}$  (because all-zero pattern cannot appear)

 
## ❑ 37-bit cellular automata shift register

- Combines previous and next statereg into current state reg
- Similar to 37 intertwined state machines (automata)
- Maximal Length:  $2^{37}-1$
- Bias  $\sim 2^{-37}$


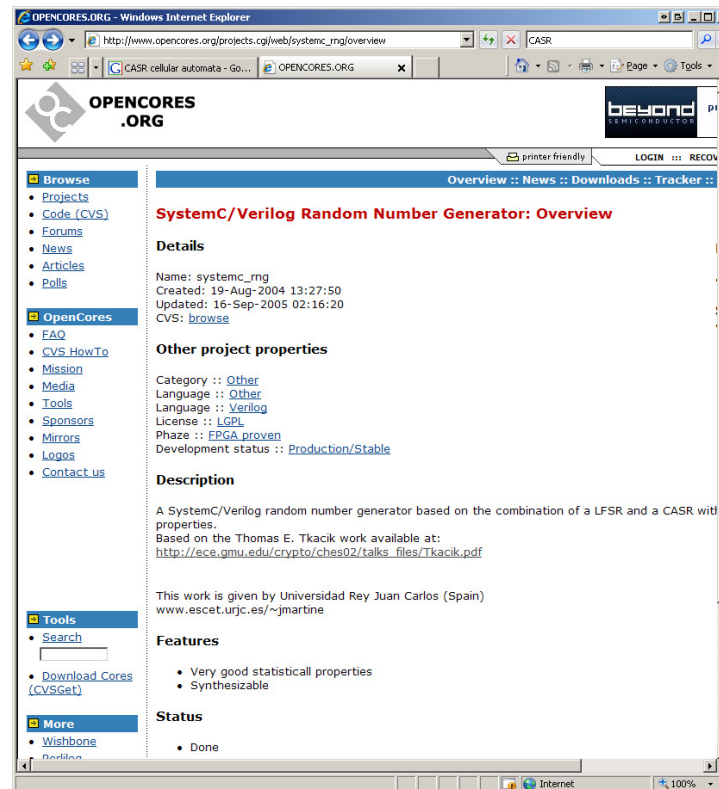
# Sample Implementation

- ❑ On opencores you can find an implementation of Tkacik's design - *assigned reading of today*
  - (this design has a few minor differences with the spec written by Tkacik - but OK for our purpose)



# Module interface

---

```
module rng(clk,reset,loadseed_i,seed_i,number_o);  
  input  clk;  
  input  reset;  
  input  loadseed_i;  
  input  [31:0] seed_i;  
  output [31:0] number_o;  
  reg    [31:0] number_o;  
  
  reg    [42:0] LFSR_reg;  // internal state  
  reg    [36:0] CASR_reg;  // internal state  
  
  always (... CASR ...)  
  
  always (... LFSR ...)  
  
  always (... combine outputs ...)  
  
endmodule
```


# LFSR Part

---

```
reg[42:0] LFSR_varLFSR; // temporary working var
reg outbitLFSR;         // temporary working var
always @(posedge clk or negedge reset)
    begin
        if (!reset )
            begin
                ...
            end
        else
            begin
                if (loadseed_i )
                    begin
                        ...
                    end
                else
                    begin
                        ...
                    end
            end
        end
    end
```
 
# LFSR Part

```
reg[42:0] LFSR_varLFSR; // temporary working var
reg outbitLFSR;         // temporary working var
always @(posedge clk or negedge reset)
    begin
        if (!reset )
            begin
                LFSR_reg = (1);
            end
        else
            begin
                if (loadseed_i )
                    begin
                        LFSR_varLFSR [42:32]=0;
                        LFSR_varLFSR [31:0]=seed_i ;
                        LFSR_reg  = (LFSR_varLFSR );
                    end
                else
                    begin
                        ...
                    end
            end
    end
end
```




# LFSR Part

```

reg [42:0] LFSR_varLFSR; // temporary working var
reg outbitLFSR;          // temporary working var
always @(posedge clk or negedge reset)
    begin
        if (!reset )
        else
            begin
                if (loadseed_i )
                else
                    begin
                        LFSR_varLFSR = LFSR_reg;
                        LFSR_varLFSR [42] = LFSR_varLFSR [41];
                        outbitLFSR      = LFSR_varLFSR [42];
                        LFSR_varLFSR [42] = LFSR_varLFSR [41];
                        LFSR_varLFSR [41] = LFSR_varLFSR [40]^outbitLFSR ;
                        // some lines skipped ...
                        LFSR_varLFSR [0]  = LFSR_varLFSR [42];
                        LFSR_reg          = LFSR_varLFSR;
                    end
                end
            end
        end
    end

```

 



# CASR Part (similar ...)

---

```
//CASR:
reg[36:0] CASR_varCASR,CASR_outCASR;
always @(posedge clk or negedge reset)
begin
    if (!reset )
        begin
            ...
        end
    else
        begin
            if (loadseed_i )
                begin
                    ...
                end
            else
                begin
                    ...
                end
        end
    end
end
```

# CASR Part (similar ...)

---

```
//CASR:
reg[36:0] CASR_varCASR, CASR_outCASR; // temp
always @(posedge clk or negedge reset)
begin
    if (!reset )
        begin
            CASR_reg = 1;
        end
    else
        begin
            if (loadseed_i )
                begin
                    CASR_varCASR [36:32]= 0;
                    CASR_varCASR [31:0] = seed_i ;
                    CASR_reg  = (CASR_varCASR );
                end
            else
                begin
                    ...
                end
            end
        end
    end
end
```

# CASR Part (similar ...)

---


```
//CASR:
reg[36:0] CASR_varCASR,CASR_outCASR; // temp
always @(posedge clk or negedge reset)
    begin
        if (!reset )
        else
            begin
                if (loadseed_i )
                else
                    begin
                        CASR_varCASR      = CASR_reg ;
                        CASR_outCASR [36]= CASR_varCASR [35]^CASR_varCASR [0];
                        CASR_outCASR [35]= CASR_varCASR [34]^CASR_varCASR [36];
                        // ... some lines skipped
                        CASR_reg          = CASR_outCASR;
                    end
                end
            end
        end
```

# Combine outputs



---

```
always @(posedge clk or negedge reset)
begin
  if (!reset )
    begin
      number_o  = (0);
    end
  else
    begin
      number_o  = (LFSR_reg [31:0]^CASR_reg[31:0]);
    end
  end
```

# Simulation ..

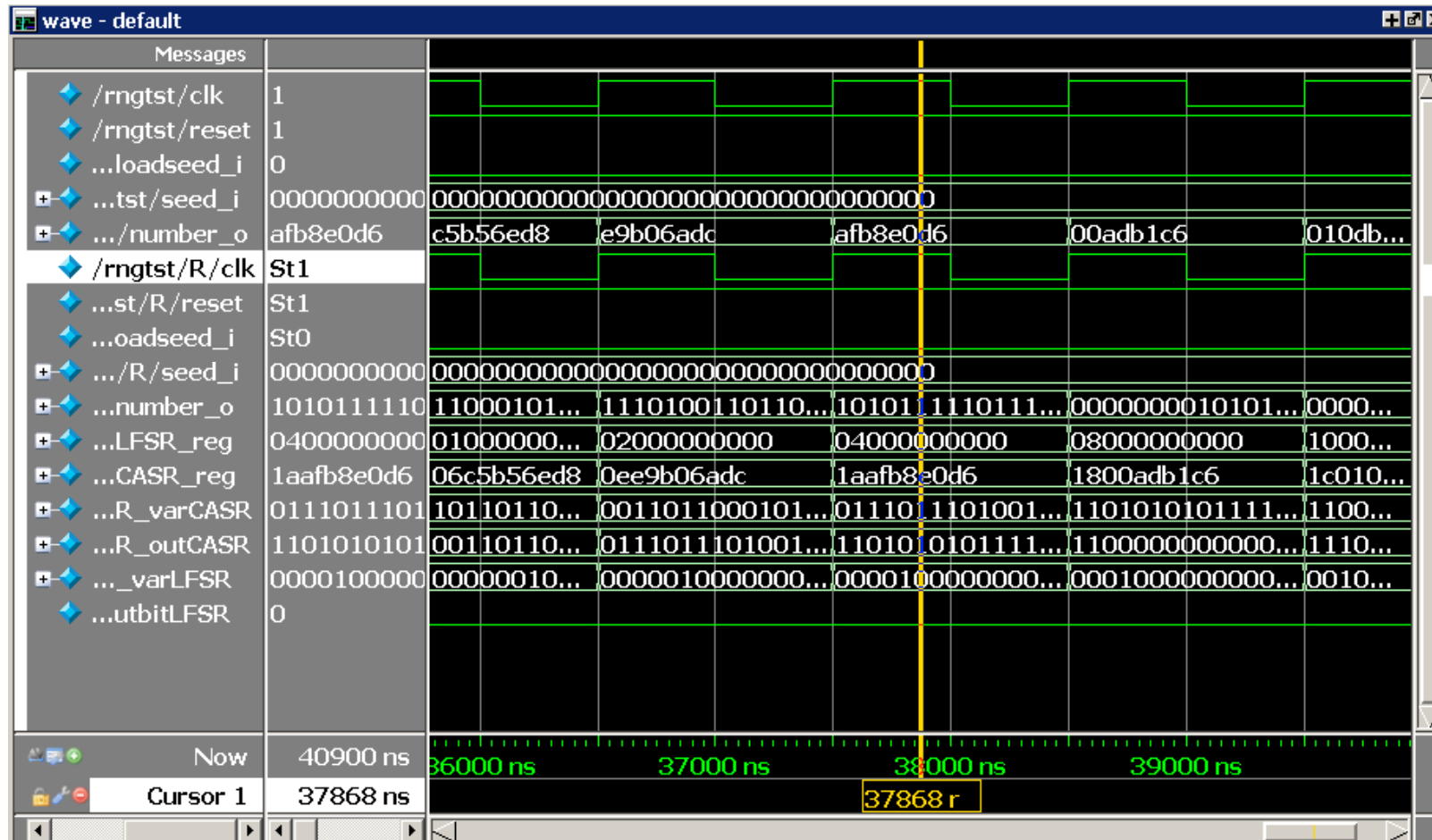

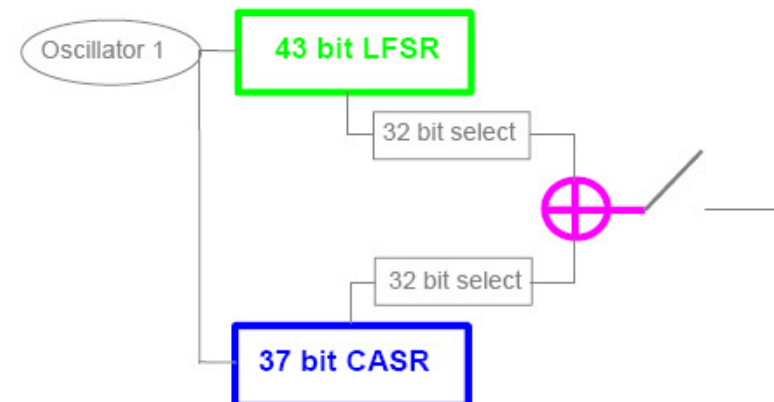 
# Simulation (looking at the state registers)




# Synthesis ..

---

 

# Place and Route ..

---

 



# Summary

---

- ❑ Random number generators
  - Many useful applications
- ❑ Linear Feedback Shift Registers: PRNG
  - Fibonacci and Galois
  - Maximal-length LFSR
  - Structural Verilog Model
- ❑ Flaws of Random Number Generators
  - Bias
  - Predictability
- ❑ Nonlinear Combination Generator
  - Design by Tkacik
  - Behavioral Verilog Model